 


Finite State Machines


We are going to design Moore and Mealy state machines for detection of *overlapping* sequence 101.

Moore State Machine



It can be coded as shown in Listing 1.

Mealy State Machine

 

It can be coded as shown in Listing 2.

```

module stg101(
    input logic clk,
    input logic reset,
    input logic in,
    output logic out );

    logic [1:0] c_state, n_state;
    parameter S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11;

    //state register
    always_ff @ (posedge clk or negedge reset)
    begin
        //reset is active low
        if (!reset)
            c_state <= S0;
        else
            c_state <= n_state;
        end

    //next_state always block
    always_comb
    begin
        case (c_state)
        S0: begin if (in) n_state = S1;
                else n_state = S0; end
        S1: begin if (in) n_state = S1;
                else n_state = S2; end
        S2: begin if (in) n_state = S3;
                else n_state = S0; end
        S3: begin if (in) n_state = S1;
                else n_state = S2; end

        default: n_state = S0;
        endcase
    end

    //output always block
    always_comb
    begin
        case (c_state)
        S0: out = 1'b0;
        S1: out = 1'b0;
        S2: out = 1'b0;
        S3: out = 1'b1;
        default: out = 1'b0;
        endcase
    end
endmodule

```

Listing 1: System Verilog Code for Moore STG

```

module stg101(
input logic clk,
input logic reset,
input logic in,
output logic out );

logic [1:0] c_state, n_state;
parameter S0=2'b00, S1=2'b01, S2=2'b10;

//state register
always_ff @ (posedge clk or negedge reset)
begin
//reset is active low
if (!reset)
c_state <= S0;
else
c_state <= n_state;
end

//next_state always block
always_comb
begin
case (c_state)
S0: begin if (in) n_state = S1;
else n_state = S0; end

S1: begin if (in) n_state = S1;
else n_state = S2; end

S2: begin if (in) n_state = S1;
else n_state = S0; end

default: n_state = S0;
endcase
end

//output always block
always_comb
begin
case (c_state)
S0: begin if (in) out = 1'b0;
else out = 1'b0; end

S1: begin if (in) out = 1'b0;
else out = 1'b0; end

S2: begin if (in) out = 1'b1;
else out = 1'b0; end

default: out = S0;
endcase
end
endmodule

```

Listing 2: System Verilog Code for Mealy STG